


Remember in *ANNA* there are 16 instruction bits, with each instruction type having unique splits.

Instruction Formats



Instructions adhere to one of the following three instruction formats:

I6-type (addi, shf, lw, sw)									
15	12	11	9	8	6	5			0
Opcode		<i>R_D</i>		<i>R_S</i>		Imm6			

I8-type (lli, lui, beq, bne, bgt, bge, blt, bbe)									
15	12	11	9	8	7				0
Opcode		<i>R_D</i>		Unused		Imm8			


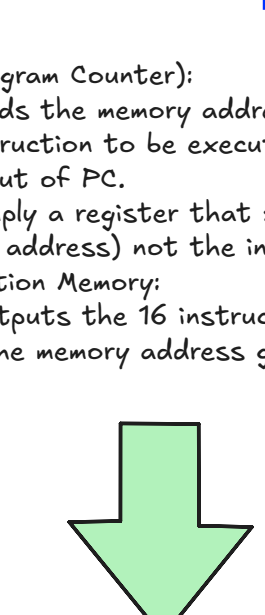


PC (Program Counter):
- Holds the memory address of the next instruction to be executed. Addr is the output of PC.
- Simply a register that stores a number (the address) not the instruction itself.
Instruction Memory:
- Outputs the 16 instruction bits (in *ANNA*) at the memory address given by PC.

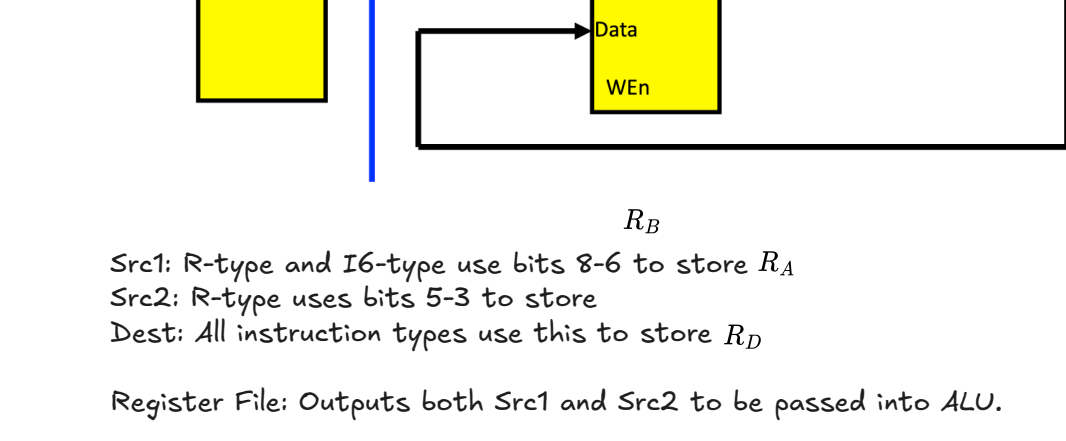 


Src1: R-type and I6-type use bits 8-6 to store *R_A*
Src2: R-type uses bits 5-3 to store *R_B*
Dest: All instruction types use this to store *R_D*

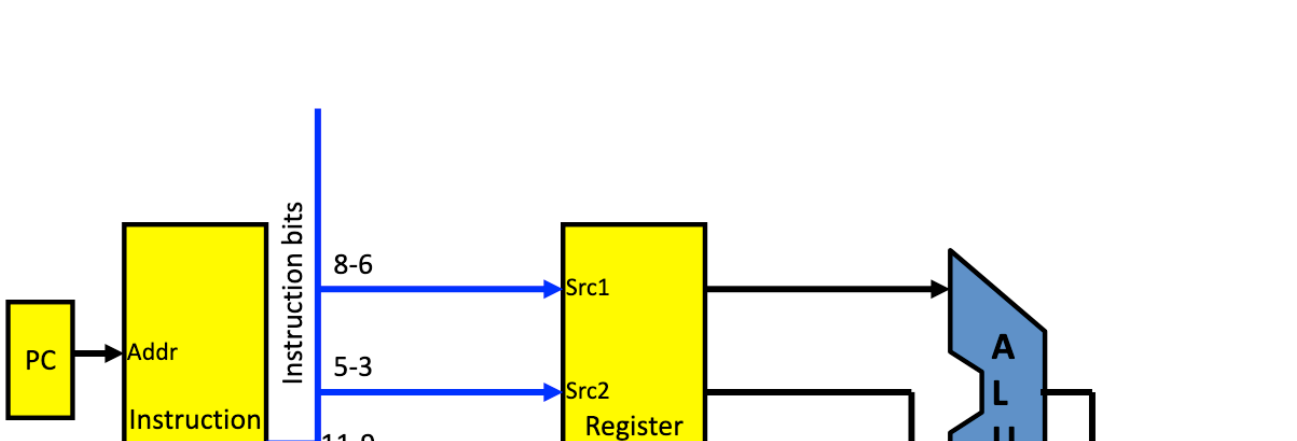 
Register File: Outputs both Src1 and Src2 to be passed into ALU.



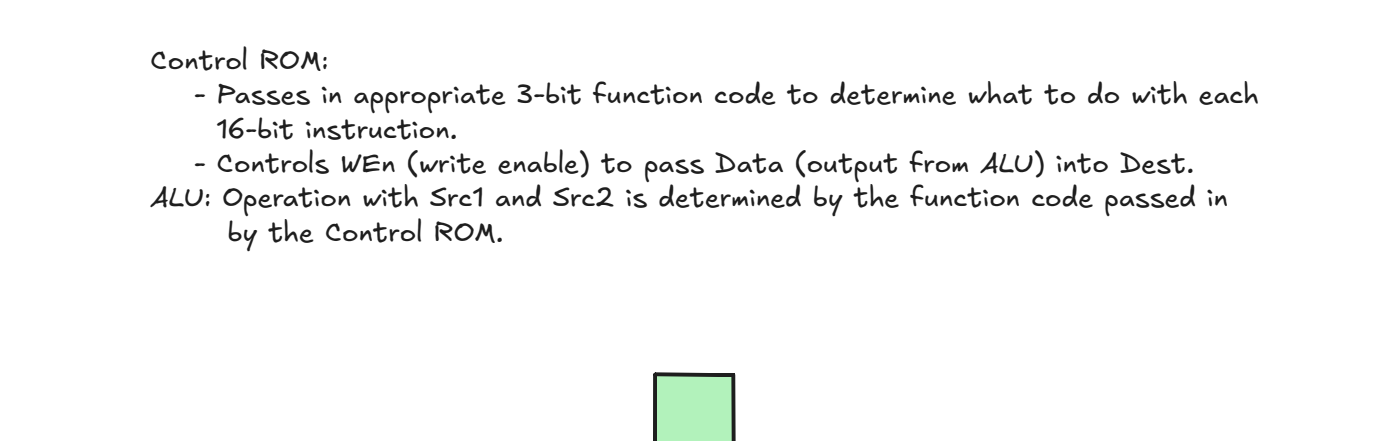Control ROM:
- Passes in appropriate 3-bit function code to determine what to do with each 16-bit instruction.
- Controls WEn (write enable) to pass Data (output from ALU) into Dest.
ALU: Operation with Src1 and Src2 is determined by the function code passed in by the Control ROM.



 Adder: Increments PC by one word (since *ANNA* is word-Addressable)




Sign Extension: When I6-type is used sign extension is used to turn that Imm6 -> Imm16.
Multiplexer: Control ROM will know if this is I6-type and will use sign extension output if this is the case. Then, will pass output into ALU.



When I6-type: passes in *R_A* and Imm6 to ALU.

When R-type: passes in *R_A* and *R_B* to ALU.

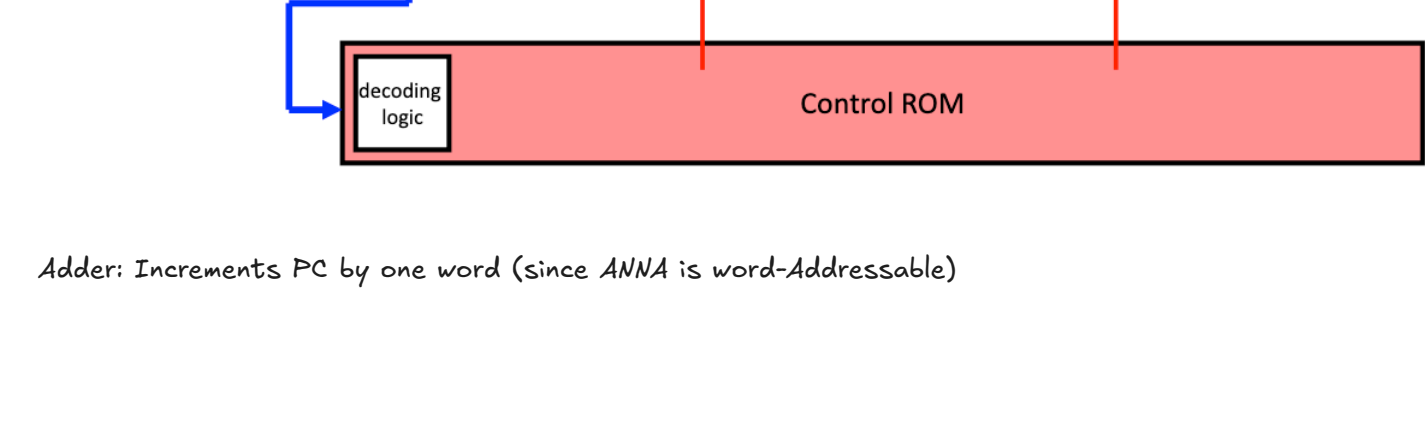Note: This multiplexer strategy will be used in a similar fashion later on to help us handle different types.





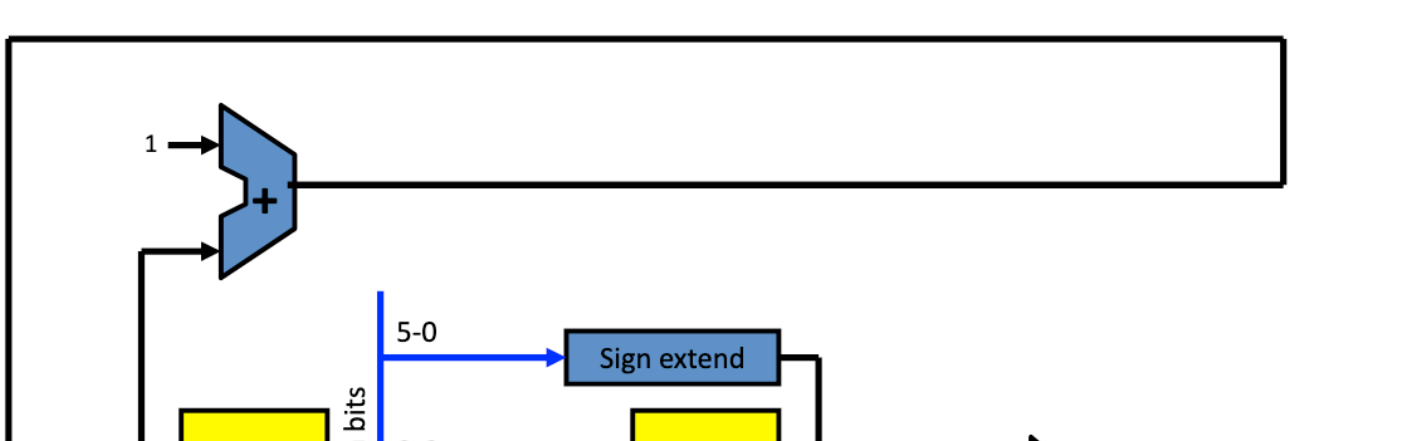 When I8 type:
- Sign Extend will extend Imm8 -> Imm16
- Multiplexer will pass this Imm16 into ALU (we will see that Src1 is changed in next part, since *R_A* is not used in I8-type).




New Multiplexers:
- 11-9 & 8-6 MUX: Separates R-type & I6-type from I8-type (since I8-type does NOT use *R_A*).
- 11-9 & 5-3 MUX: Separates I6-type & I8-type from R-type (since only R-type uses *R_B*).
Data Memory: Used for lw (load word) and sw (store word) instructions (in *ANNA*). Address will be output of ALU with input *R_A* and Imm6. Data will be stored in *R_D*.

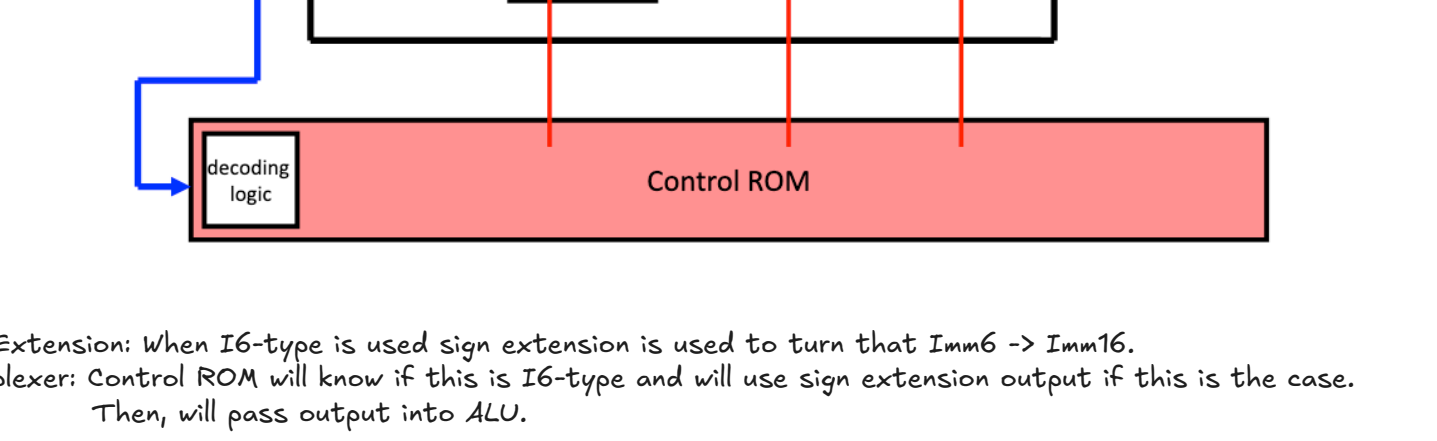 - Remember:
- ONLY Enabled when lw is called



 New Multiplexer: Handles what should be placed in the data register *R_D*.
Either from the output of the ALU or straight from Data Memory.



Branch detection: Checks for branch instruction (i.e. beq, bne, bgt, etc.), passes 1 into MUX if instruction is a branch.